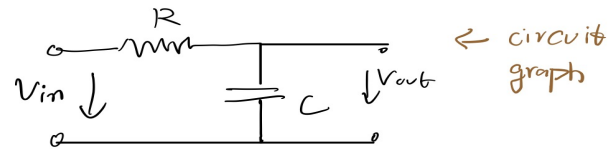


R4.1

Passive analog LP filter Design

R4.1



$$\left| \frac{V_{out}}{V_{in}} \right|^2 = \frac{\left(\frac{1}{2\pi f C} \right)^2}{\left(\frac{1}{2\pi f C} \right)^2 + R^2}$$

cut-off frequency $f_c = \frac{1}{2\pi R C}$, $\frac{V_{out}}{V_{in}} = \frac{1}{\sqrt{2}}$

$$R = \frac{1}{2\pi f_c C}$$

suppose $R = 1k\Omega$, $f_c = 50Hz$

$$C = \frac{1}{2\pi R f_c} = 3.18 \times 10^{-6} F$$

•

R4.2

R 4.2 discrete LP filter Design

$$\frac{V_y(s)}{V_x(s)} = \frac{\frac{1}{sC}}{R + \frac{1}{sC}}$$

$$H(s) = \frac{1}{sCR + 1}$$

according to the
analog filter we get

$$K = CR = \frac{1}{2\pi f_c}$$

$$H(z) = \frac{1}{\frac{2}{T} \frac{z-1}{z+1} K + 1}$$

using bilinear transformation

$$s = \frac{2}{T} \left[\frac{z-1}{z+1} \right]$$

$$= \frac{(z+1)}{\frac{2}{T} (z-1)K + (z+1)}$$

$$= \frac{(z+1)}{(K \frac{2}{T} + 1)z - (K \frac{2}{T} - 1)}$$

$$\text{zero} = -1$$

$$\text{pole} = \frac{K \frac{2}{T} + 1}{K \frac{2}{T} - 1} = 0.9691$$

Implementation on data stream
According to the following formula

$$\sum_{i=0}^p a_i y(n-i) = \sum_{i=0}^q b_i x(n-i)$$

$$p=q=1 \quad \frac{0.0155z + 0.0155}{z + (-0.9691)} = \frac{0.0155 + 0.0155z^{-1}}{1 + (-0.9691)z^{-1}}$$

$$a_0 = 1 \quad a_1 = -0.9691 \quad b_0 = b_1 = 0.0155$$

The filtered data can be computed as follows

$$y(0) = x(0)$$

$$y(1) = -a_1(y(0)) + b_0 x(1) + b_1 x(0)$$


$$y(2) = -a_1(y(1)) + b_0 x(2) + b_1 x(1)$$

⋮

•

R4.3

R4.3 Design of analog HP filter

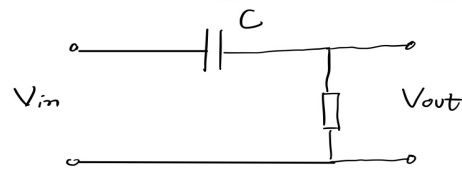

$$A = \frac{V_{out}}{V_{in}} = \frac{R}{\sqrt{R^2 + X_C^2}} = \frac{R}{\sqrt{\left(\frac{1}{2\pi f C}\right)^2 + R^2}}$$

$$A^2 = \frac{R^2}{\left(\frac{1}{2\pi f C}\right)^2 + R^2} \stackrel{!}{=} \frac{1}{2}$$

$$f_c = \frac{1}{2\pi RC}$$

$$\frac{V_{y(rs)}}{V_{x(rs)}} = \frac{R}{R + \frac{1}{sC}}$$

$$H(s) = \frac{sCR}{sCR + 1}$$

cut-off frequency $f_c = \frac{1}{2\pi RC}$, $\frac{V_{out}}{V_{in}} = \frac{1}{\sqrt{2}}$

$$R = \frac{1}{2\pi f_c C}$$

suppose $R = 1k\Omega$, $f_c = 500$

$$C = \frac{1}{2\pi R f_c} = 3.18 \times 10^{-7} \text{ F}$$

R4.4

R4.4 Discrete HP filter design

$$K = 0.12 = \frac{1}{2\pi f} = 3.18 \times 10^{-4}$$

using bilinear transformation

$$s = \frac{2}{T} \left[\frac{z-1}{z+1} \right]$$

$$\begin{aligned} H(z) &= \frac{\frac{2}{T} \frac{z-1}{z+1} K}{\frac{2}{T} \frac{z-1}{z+1} K + 1} \\ &= \frac{2(z-1)K}{2(z-1)K + T(z+1)} \\ &= \frac{(z-1)2K}{(2K+T)z - (2K-T)} \end{aligned}$$

$$\text{zero} = 1$$

$$\text{pole} = \frac{2K-T}{2K+T} = 0.7285$$

$$= \frac{0.8641z - 0.8641}{z - 0.7285}$$

Implementation on data stream
According to the following formula

$$\sum_{i=0}^p a_i y(n-i) = \sum_{i=0}^q b_i x(n-i)$$

$$p=q=1 \quad \frac{0.8641 z - 0.8641}{z - 0.7285}$$

$$= \frac{0.8641 - 0.8641 z^{-1}}{1 + (-0.7285) z^{-1}}$$

$$a_0 = 1 \quad a_1 = -0.7285 \quad b_0 = 0.8641 \quad b_1 = -0.8641$$

$$y(0) = x(0)$$


$$y(1) = -a_1(y(0)) + b_0 x(1) + b_1 x(0)$$

$$y(2) = -a_1(y(1)) + b_0 x(2) + b_1 x(1)$$

.

R4.5

R4.5 Analog Band pass active filter

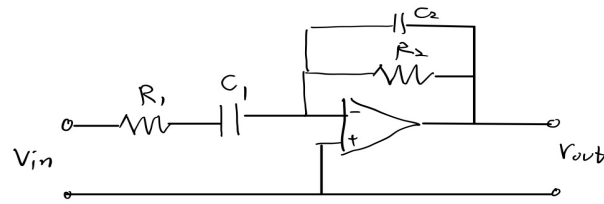

$$\frac{V_{out}}{V_{in}} = \frac{-Z_2}{Z_1} = -\frac{\frac{R_2 X_{C2}}{R_2 + X_{C2}}}{R_1 + X_{C1}}$$

$$= \frac{2\pi f C_1 R_2}{(1 + 2\pi f C_2 R_2)(1 + 2\pi f C_1 R_1)}$$

$$A^2 = \frac{1}{\Delta} \quad \downarrow$$

$$f_L = \frac{1}{2\pi R_1 C_1} \quad f_H = \frac{1}{2\pi R_2 C_2}$$

suppose $f_L = 200 \text{ Hz}$ $f_H = 800 \text{ Hz}$
 $R_1 = R_2 = 1 \text{ k}\Omega$

$$C_1 = \frac{1}{2\pi R_1 f_L} = 795 \times 10^{-7} \text{ F}$$

$$C_2 = \frac{1}{2\pi R_2 f_H} = 1.99 \times 10^{-7} \text{ F}$$

•

R4.6

R4.6 discrete bandpass filter design

$$H(s) = \frac{SC_1 R_2}{(1 + SC_1 R_1)(1 + SC_2 R_2)}$$

$$= \frac{7.95 \times 10^{-4} s}{1.55 \times 10^{-7} s^2 + 9.95 \times 10^{-4} s + 1}$$

using bilinear transform

$$H(z) = \frac{0.189 z^2 - 0.189}{z^2 - 1.48z + 0.5276}$$

$$= \frac{0.189 - 0.189 z^{-2}}{1 - 1.482 z^{-1} + 0.5286 z^{-2}}$$

$$b_0 = 0.189 \quad b_2 = -0.189$$

$$a_0 = 1 \quad a_1 = -1.482 \quad a_2 = 0.5286$$

Data stream implementation

$$y(i) = -a_1(y(i-1)) - a_2(y(i-2))$$

$$+ b_0 x(i) + b_1(x(i-1)) + b_2(x(i-2))$$

•

R4.7 What is the difference between passive and active filters?

1. Passive filter only contains passive components, such as resistors, capacitors and inductors; Active filter also uses active components such as op-amp
2. The active filter need additional power resource for active components
3. The active filter performs better with load

R4.8: What is the difference between FIR and IIR filters?

- The FIR(Finite Impulse Response) filter is implemented as the following formula:

$$y(n) = \sum_{k=0}^N a(k)x(n-k)$$

- The IIR(Infinite Impulse Response) filter can be implemented by the following formula, it is computed recursively

$$y(n) = \sum_{k=0}^N a(k)x(n-k) + \sum_{j=0}^p b(j)y(n-j)$$

- **The IIR(Infinite Impulse Response) filter** calculate the output recursively and typically sharper than FIR filter with same order. So with same performance IIR is more computational cheap. But it is less

stable. On the other hand,

- **FIR(Finite Impulse Response) filter** has the same phase delay, which can not be achieved by IIR.

R4.9: What is the “order” of a discrete filter?

- The order of discrete filter refers to the number of N in the following formula:

$$y(n) = \sum_{k=0}^N a(k)x(n-k) \quad y(n) = \sum_{k=0}^N a(k)x(n-k) + \sum_{j=0}^p b(j)y(n-j)$$

- A filter with higher order has sharper edges

R4.10: How could you implement a continuous-time filter in a robotic system?

- A continuous-time filter can be implemented with circuit components (R,C,L,op-amp).

R4.11: How could you implement a discrete-time filter in a robotic system?

- A discrete-time filter can be implemented with microcontroller, we can input the data stream and using IIR or FIR filter parameters to process them and output the result.

R4.12: What are the advantages and disadvantages of analog and digital filters in robotic systems?

- Analog filters
 1. Advantages: faster, no ADC requirement
 2. Disadvantages: additional hardware; can be affected by load, less accurate
- Discrete filters
 1. Advantages: more accurate, programmable
 2. Disadvantages: signals need to be digitalized with ADC; need additional analog filter to get rid of high frequency noise that above nyquist frequency to avoid aliasing effect.

R4.13: Is it possible to make a 1000 Hz Low-Pass filter in a digital system with a sampling rate of 1000 Hz?

- It is not possible, the 1000Hz sampling rate can only recover signal within the range (0-500Hz) because of the nyquist sampling theory.